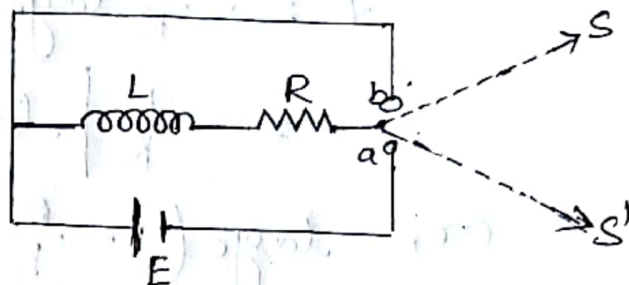


Growth of Current in L-R Circuit.

Let us consider a circuit containing an inductance L and a wire resistance R in series when a cell of constant e.m.f.



E is connected in series with it. When the circuit is closed by throwing the switch S to a point 'a' a self induction e.m.f. is set up in the coil which opposes the applied e.m.f. Hence the current does not reach its final steady value E/R instantaneously. The current grows at a rate depending upon the inductance and resistance of circuit.

Let I be the current at any instant t .

$$\therefore \text{Rate of growth of Current} = \frac{dI}{dt}$$

$$\therefore \text{Induced e.m.f. across the coil} = -L \frac{dI}{dt}$$

$$\therefore \text{Effective e.m.f.} = E - L \frac{dI}{dt}$$

But the effective e.m.f. = potential sets across the resistance $R = IR$

$$\therefore E - L \frac{dI}{dt} = RI$$

$$\therefore E - RI = L \frac{dI}{dt}$$

$$\therefore dt = \frac{L dI}{E - RI}$$

$$\int dt = \frac{L}{E - RI} \int dI$$

$$\text{or, } t = -\frac{L}{R} \log_e(E - RI) + C \quad \text{--- (1)}$$

where C is a constant of integration At $t=0, I=0$

$$\therefore C = \frac{L}{R} \log_e(E)$$

\therefore from equation (1) we have

$$t = -\frac{L}{R} \log_e(E - RI) + \frac{L}{R} \log_e(E)$$

$$= -\frac{L}{R} \left[\log_e\left(\frac{E - RI}{E}\right) \right]$$

$$\text{or, } \log_e\left(1 - \frac{R}{E} \cdot I\right) = -\frac{R}{L} \cdot t$$

$$\text{or, } 1 - \frac{RI}{E} = e^{-\frac{R}{L} \cdot t}$$

$$\text{or, } \frac{RI}{E} = 1 - e^{-(R/L)t}$$

$$\therefore I = \frac{E}{R} \left(1 - e^{-(R/L)t}\right)$$

$$I = I_0 \left(1 - e^{-(R/L)t}\right) \quad \text{--- (2)}$$

This equation shows that the Current in the circuit rises according to an exponential law as shown in figure.

Differentiating eqn (2)

$$\frac{dI}{dt} = -I_0 \left(-\frac{R}{L}\right) e^{-(R/L)t}$$

$$= I_0 \left(\frac{R}{L}\right) e^{-(R/L)t}$$

From equation (2)

$$\frac{I}{I_0} = 1 - e^{-(R/L)t}$$

$$\text{or, } e^{-(R/L)t} = \left(\frac{I_0 - I}{I_0}\right), \therefore \frac{dI}{dt} = I_0 \left(\frac{I - I_0}{I_0}\right) \frac{R}{L} = \frac{R}{L} (I - I_0) \quad \text{--- (3)}$$

This is clear that the rate of growth of Current depends only the value of R/L . The quantity L/R is called the time constant of the circuit and is denoted by λ .

$$\therefore \lambda = \frac{L}{R}$$

from eqn (2) we have, $I = I_0 \left(1 - e^{-t/\lambda}\right) \quad \text{--- (4)}$

